

Module 2 BASIC ELECTRIC

Name:

Date:


Part A: Multiple choice question (MCQ)

- | | |
|---|---|
| <p>1) The symbol unit for resistance is.</p> <p>(a) F
(b) A
(c) W
(d) Ω</p> <p>2) What is the unit for power?</p> <p>(a) volts
(b) ampere
(c) watts
(d) volt-ampere</p> <p>3) A resistance of an electric fan is 420 Ω and operating current at 2.4 ampere, calculate the power in watts?</p> <p>(a) 2280.2 w
(b) 2300.2 w
(c) 2419.2 w
(d) 2820.2 w</p> <p>4) The total voltage of each resistor R1 and R2 in parallel circuits is _____.</p> <p>(a) to be add (R1+R2)
(b) the same
(c) R1 is bigger then R2
(d) R1 is smaller than R2</p> <p>5) In series circuits when two or more resistor is connected, the value of the current is.</p> <p>(a) is small
(b) is bigger
(c) remain the same
(d) voltage is higher</p> | <p>6) What is the angle differences between red and yellow phase in three phase system?</p> <p>(a) 90°
(b) 180°
(c) 120°
(d) 360°</p> <p>7) A water heater rated 3200 watt operate at 240 volt, calculate the operating current?</p> <p>(a) 13.33 ampere
(b) 23.33 ampere
(c) 33.33 ampere
(d) 34.33 ampere</p> <p>8) What is the value of V_{rms} if 240v supply?</p> <p>(a) 169.68 volt
(b) 125.68 volt
(c) 220.68 volt
(d) 340.68 volt</p> <p>9) What is the value of voltage average (V_{avg}) when V_p is 220v supply?</p> <p>(a) 98.5 volt
(b) 125.8 volt
(c) 133.7 volt
(d) 140.58 volt</p> <p>10) A capacitor is device capable to_____.</p> <p>(a) store energy charge
(b) store current
(c) store power
(d) store resistance</p> |
|---|---|

- 11) What is the unit for apparent power?
- (a) ampere
 - (b) watts
 - (c) volt-ampere
 - (d) volt-ampere reactive
- 12) The value of power factor is 0.78, calculate the angle in degree.
- (a) 19°
 - (b) 26°
 - (c) 38°
 - (d) 42°
- 13) What is the ideal value of power factor according to requirement?
- (a) <0.65 or smaller
 - (b) <0.85 or smaller
 - (c) >0.55 or greater
 - (d) >0.85 or greater
- 14) The following are the resistive loads, except.
- (a) electronic
 - (b) heater unit
 - (c) motor electric
 - (d) emergency light
- 15) The following is the cause of low power factor, except.
- (a) electric motor
 - (b) rectifier DC circuit
 - (c) transformer
 - (d) fan or blower
- 16) A ballast is labelled 0.38 henry and frequency is 50 Hertz, calculate the inductive reactance (XL)?
- (a) 58.55Ω
 - (b) 85.35Ω
 - (c) 119.32Ω
 - (d) 145.55Ω
- 17) A capacitor is $100\mu\text{F}/220\text{VAC}$ and frequency is 50 Hertz, calculate the capacitive reactance (Xc)?
- (a) 18.45Ω
 - (b) 25.75Ω
 - (c) 31.84Ω
 - (d) 44.25Ω
- 18) What is the out wave form produced after rectifier and filtered
- (a) square wave
 - (b) sine wave
 - (c) saw tooth wave
 - (d) direct straight line
- 19) What is the function of rectifier device in the DC supply?
- (a) to lower the voltage
 - (b) to change volts into ampere
 - (c) to limit the current flow
 - (d) to change voltage from AC to DC
- 20) The transformer is one of the component inside the DC supply power, what is the function for this device?
- (a) to store current
 - (b) to lower voltage
 - (c) to store power
 - (d) to increase voltage

Part B: Subjective Question

1)

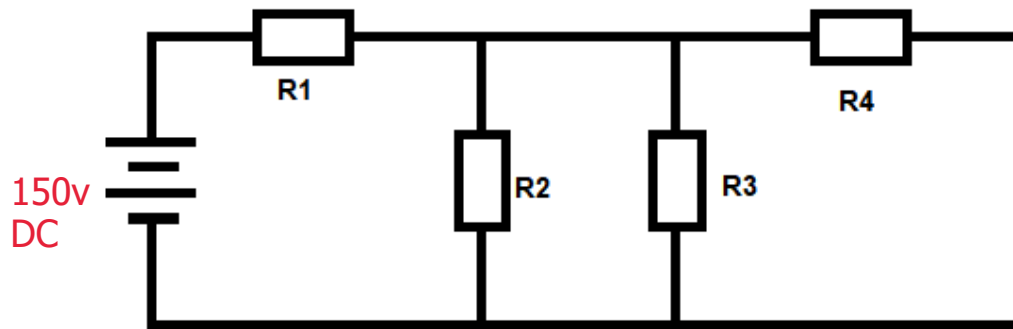


Refer to figure above is a series-parallel circuit, calculate the following values required. Given value $R1=250\Omega$, $R2=380\Omega$, $R3=120\Omega$ and $R4=320\Omega$.

a) Find resistance total, R_t ?

b) Calculate the current total, I_t ?

c) Calculate the voltage across $R3$ and $R4$?

2)

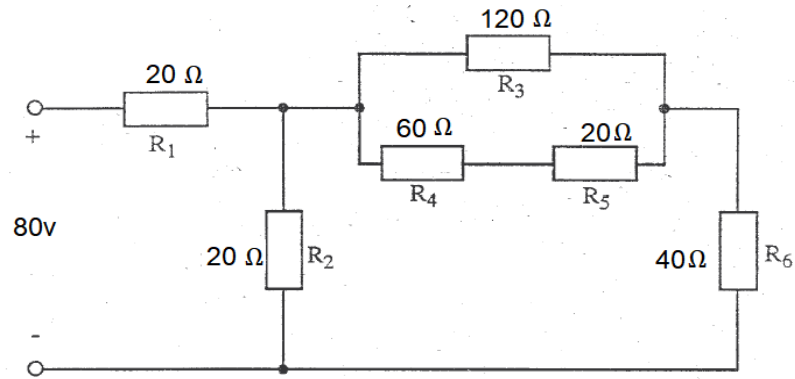

Refer to figure above calculate the required values.

a) Find resistance total, R_t ?

b) Calculate the current total, I_t ?

3)



Refer to figure above calculate the required values.

Given value of $R=60\Omega$, $L=0.35H$, $C=88.46\mu F$ and $Freq=50Hz$.

a) find impedance Z ?

b) calculate the power factor

c) find the angle of \cos in degree.

- 4) a) A building operates on the total load is 55.6 kW, the power factor is set at 0.86, calculate the apparent power, S?
- b) A machine draws about 75.8 ampere current and operates on 415 volt supply.
- i) Calculate the true power, P.
- ii) If the apparent power S (design power) is 61,914.9 VA, calculate the power factor?
- c) Given the apparent power S=70 kVA and true power P=58 kW, calculate the reactive power, Q?
- 5) a) List down four (4) dis-advantage of low power factor.
- i)
- ii)
- iii)
- iv)
- b) List down three (3) magnetism material.
- i)
- ii)
- iii)
- c) Write down the correct three power formula.
- i) apparent power, S
- ii) reactive power, Q
- i) power factor, (p.f)