Module 7

Name:	Date:

Part A: Multiple choice question (MCQ)


- Below are the applications for indoor lighting, except.
 - (a) task lighting
 - (b) halogen bulb
 - (c) ambient lighting
 - (d) accent lighting
- 2) This lighting is commonly operate during the night in a garden compound, which is correct?
 - (a) beacon light
 - (b) flood light
 - (c) perimeter light
 - (d) gardening light
- 3) Another name for halogen lamp is also known as.
 - (a) led lamp
 - (b) tungsten halogen lamp
 - (c) filament lamp
 - (d) discharge lamp
- 4) The white powder inside the florescent lamp is known as.
 - (a) mercury lead
 - (b) argon
 - (c) magnesium oxide
 - (d) phosphor
- 5) What is ballast factor?
 - (a) light output with a test ballast.
 - (b) inductive factor
 - (c) ballast voltage
 - (d) ballast power

- 6) What is the function of ballast in lighting?
 - (a) to increase brightness of light
 - (b) to increase voltage
 - (c) to increase electron flow
 - (d) to improve power factor
- 7) What is the role of capacitor inside a discharge lamp?
 - (a) increase the current of lamp
 - (b) increase the power of the lamp
 - (c) improve brightness of the lamp
 - (d) improve power factor
- 8) Street lighting most commonly using these types of lamp, except.
 - (a) halogen lamp
 - (b) LED lamp
 - (c) mercury lamp
 - (d) sodum lamp
- 9) What is the used of beacon lights on buildings?
 - (a) for lighting up the building at night
 - (b) for decoration purpose
 - (c) for identify building
 - (d) for planes and helicopter navigation
- 10) What is halogen lamp applications?
 - (a) for office works
 - (b) for toilet
 - (c) for bed room
 - (d) for decorative purpose

- 11) List below are the type of ballast, except.
 - (a) electronic ballast
 - (b) programmed start
 - (c) rapid start
 - (d) starter
- 12) What is the function of ignitor inside a discharge lamp?
 - (a) improve power factor
 - (b) act as starter
 - (c) increase voltage supply
 - (d) increase current higher
- 13) Control on street lighting can be applied according to list below, except.
 - (a) emergency stop button
 - (b) by time clock
 - (c) photocell (light) sensor
 - (d) direct switch
- 14) The component of solar powered lamp is list below, except.
 - (a) photovoltaic cell
 - (b) inverter
 - (c) ignitor
 - (d) rectifier circuit
- 15) What is the function of photovoltaic cell?
 - (a) to increase power of light
 - (b) to regulate the voltage
 - (c) to receive sunlight and convert into electrical energy
 - (d) to receive sunlight and convert into light energy

- 16) A compact florescent lamp is also known as.
 - (a) discharge lamp
 - (b) energy saving lamp
 - (c) mercury lamp
 - (d) sodium lamp
- 17) What is the life span of a compact florescent lamp?
 - (a) 1,500 to 3000 hours
 - (b) 4,000 to 6000 hours
 - (c) 6,000 to 10,000 hours
 - (d) 10,000 to 12,000 hours
- 18) What is the number 4 line in LT overhead line used for?
 - (a) act as power line
 - (b) act as switch wire
 - (c) act as phase distribution
 - (d) act as neutral line
- 19) The followings are the applications of solar lamp, except.
 - (a) street lighting
 - (b) gardening lighting
 - (c) indoor lighting
 - (d) parking

20)

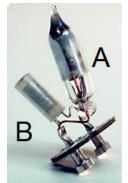

Refer to picture above, what is A?

- (a) diode
- (b) resistor
- (c) inductor
- (d) capacitor

Part B: Subjective Question

1)	List down three (3) advantage of compact florescent lamp.
	i)
	ii)
	iii)
2)	List down four (4) component inside a discharge lamp.
	i)
	ii)
	iii)
	iv)
3)	List three (3) advantage of mercury lamp.
	i)
	ii)
	iii)
4)	Draw the wiring diagram of a florescent lamp.

5) Draw the wiring diagram of a sodium discharge lamp.

Answer scheme part A objective

Part A: MCQ

1) B	6) C	11) D	16) B
2) D	7) D	12) B	17) D
3) B	8) A	13) A	18) B
4) D	9) D	14) C	19) C
5) A	10) D	15) C	20) D